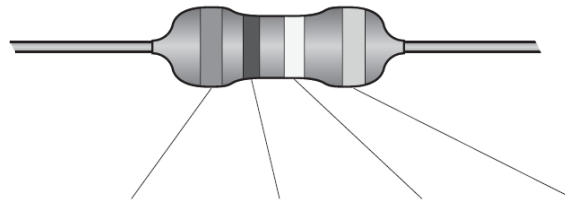


# Practical Electronics - Resistors





You will need this information to answer question 1

4-band Resistor



Colour	1st band value	2nd band value	Multiplier	Tolerances
Black	0	0	$\times 1$	
Brown	1	1	$\times 10$	$\pm 1\%$
Red	2	2	$\times 100$	$\pm 2\%$
Orange	3	3	$\times 1000$	$\pm 3\%$
Yellow	4	4	$\times 10000$	$\pm 4\%$
Green	5	5	$\times 100000$	$\pm 0.5\%$
Blue	6	6	$\times 1000000$	$\pm 0.25\%$
Violet	7	7	$\times 10000000$	$\pm 0.10\%$
Grey	8	8	$\times 100000000$	$\pm 0.05\%$
White	9	9	$\times 1000000000$	
Gold			$\times 0.1$	$\pm 5\%$
Silver			$\times 0.01$	$\pm 10\%$
No band				$\pm 20\%$

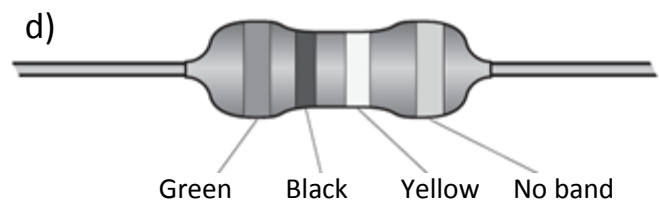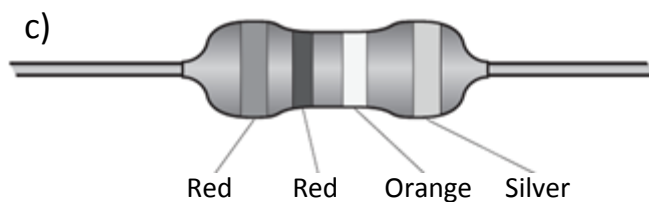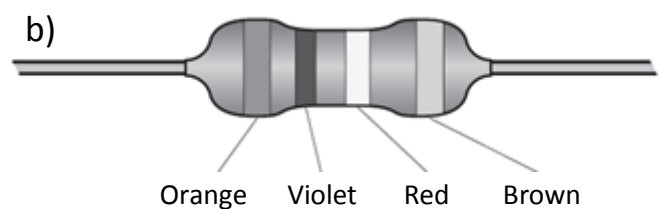
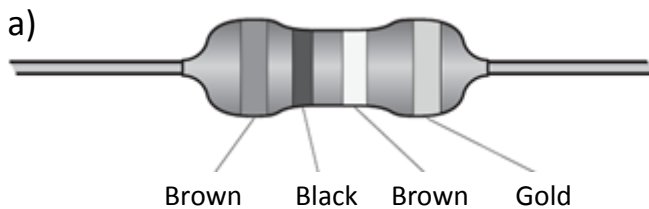
1. Determine the resistance and tolerance of each resistor shown below.



2. For each resistor above determine the maximum and minimum resistance of the resistor using the tolerance values from question 1. [8]




3. For each resistor above write down its resistance in B.S. notation. [4]

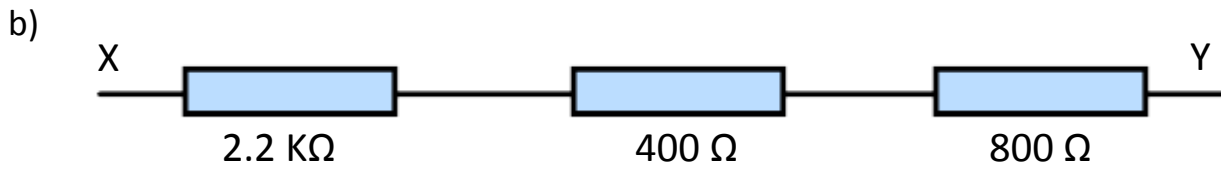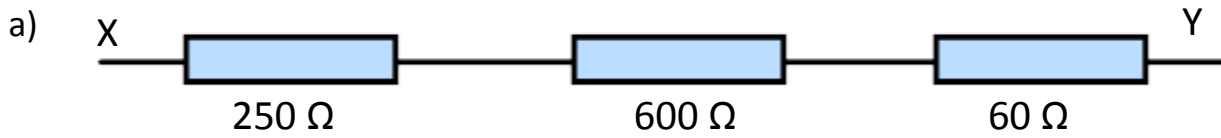4. Calculate the total resistance between X and Y for the questions below;



[4]

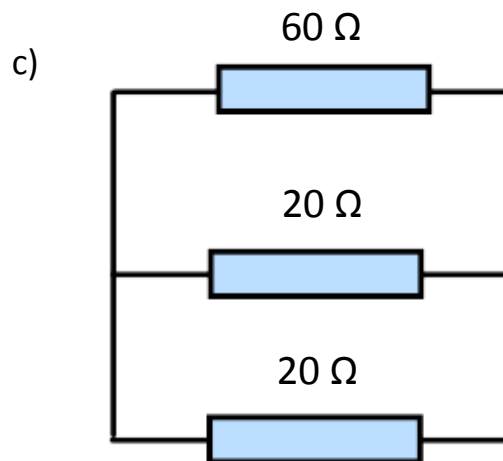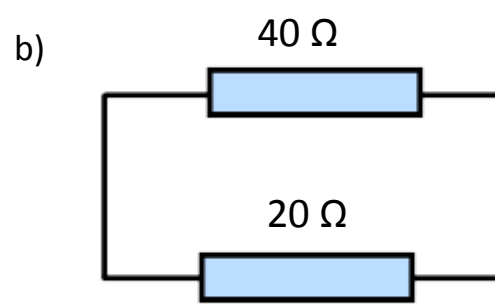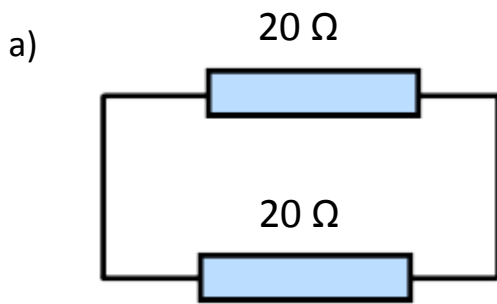5. Calculate the effective resistance of the resistors in parallel for the questions below;



[9]

Total of 25 Marks