

Exercise 13 - Capacitance

Past Paper Homework Questions

1. The unit for capacitance can be written as

A V C^{-1}

B C V^{-1}

C J s^{-1}

D C J^{-1}

E J C^{-1} .

2. A $25.0\ \mu\text{F}$ capacitor is charged until the potential difference across it is $500\ \text{V}$.

The charge stored in the capacitor is

A $5.00 \times 10^{-8}\ \text{C}$

B $2.00 \times 10^{-5}\ \text{C}$

C $1.25 \times 10^{-2}\ \text{C}$

D $1.25 \times 10^4\ \text{C}$

E $2.00 \times 10^7\ \text{C}$.

3. In an experiment to find the capacitance of a capacitor, a student makes the following measurements.


potential difference across capacitor = $(10.0 \pm 0.1)\ \text{V}$

charge stored by capacitor = $(500 \pm 25)\ \mu\text{C}$


Which row in the table gives the capacitance of the capacitor and the percentage uncertainty in the capacitance?

	<i>Capacitance/μF</i>	<i>Percentage uncertainty</i>
A	0.02	1
B	0.02	5
C	50	1
D	50	5
E	5000	6

4. A circuit is set up as shown.

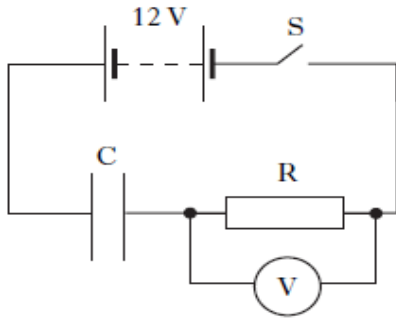

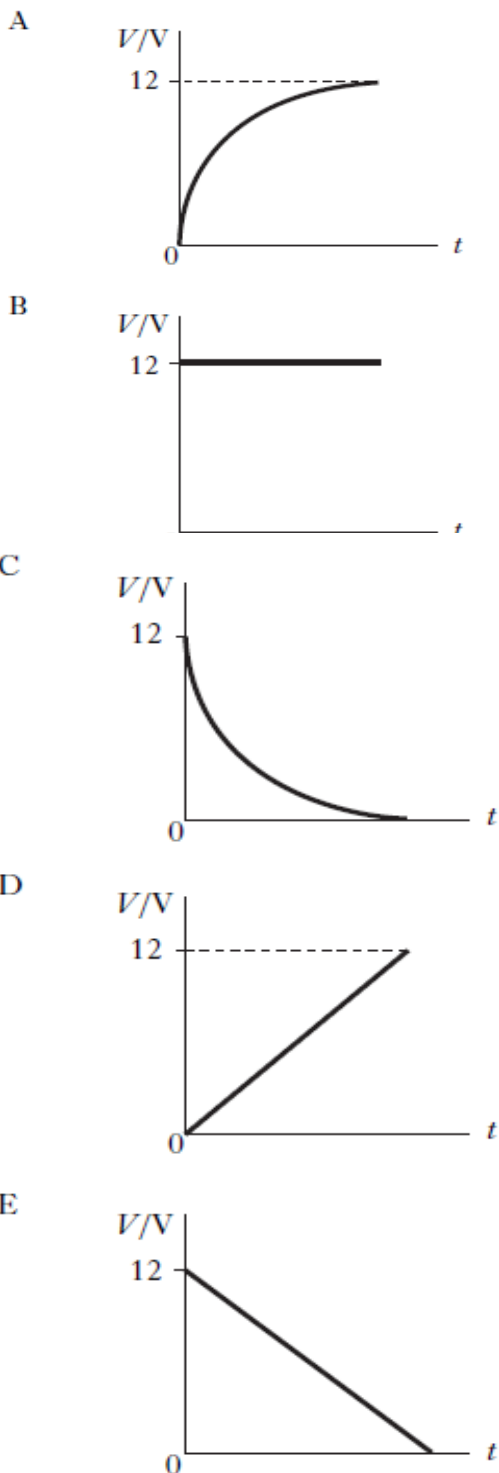The capacitor is initially uncharged. Switch S is now closed. Which graph shows how the potential difference, V , across R, varies with time, t ?



5. A student carries out an experiment to find the capacitance of a capacitor. The charge on the capacitor is measured for different values of p.d. across the capacitor. The results are shown.


charge on capacitor/ μC	p.d. across capacitor/V
1.9	1.0
4.6	2.0
9.6	4.0

The best estimate of the capacitance is

- A $1.9\ \mu\text{F}$
 B $2.2\ \mu\text{F}$
 C $2.3\ \mu\text{F}$
 D $2.4\ \mu\text{F}$
 E $2.6\ \mu\text{F}$.
6. The capacitance of a capacitor is $1000\ \mu\text{F}$. The potential difference (p.d.) across the capacitor is $100\ \text{V}$. The charge stored by the capacitor is $0.10\ \text{C}$.
- The charge on the capacitor is now reduced to half its original value.
- Which row in the table shows the capacitance of the capacitor and the p.d. across the capacitor, for this new value of charge?

	Capacitance/ μF	p.d./V
A	1000	200
B	500	100
C	1000	100
D	500	50
E	1000	50

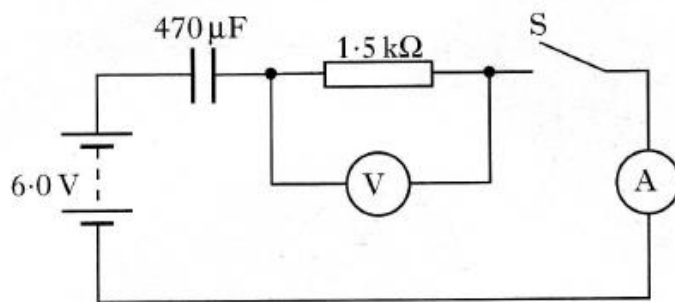7. (a) The following diagram shows a circuit that is used to investigate the charging of a capacitor.




The capacitor is initially uncharged.

The capacitor has a capacitance of $470\ \mu\text{F}$ and the resistor has a resistance of $1.5\ \text{k}\Omega$.


The battery has an e.m.f. of 6.0 V and negligible internal resistance.

- | | |
|---|---|
| (i) Switch S is now closed. What is the initial current in the circuit? | 3 |
| (ii) How much energy is stored in the capacitor when it is fully charged? | 3 |
| (iii) What change could be made to this circuit to ensure that the same capacitor stores more energy? | 1 |

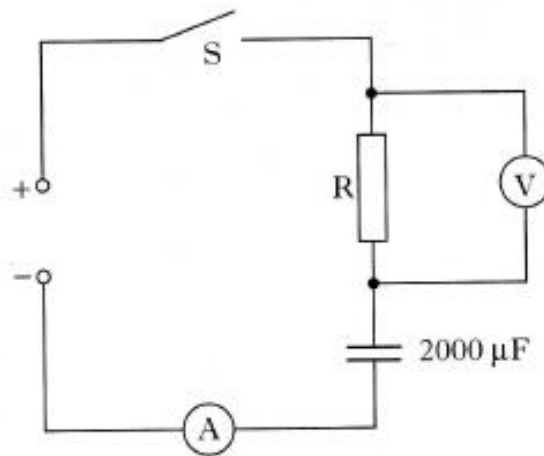8. (a) The circuit below is used to investigate the charging of a $2000\ \mu\text{F}$ capacitor. The d.c. supply has negligible internal resistance.



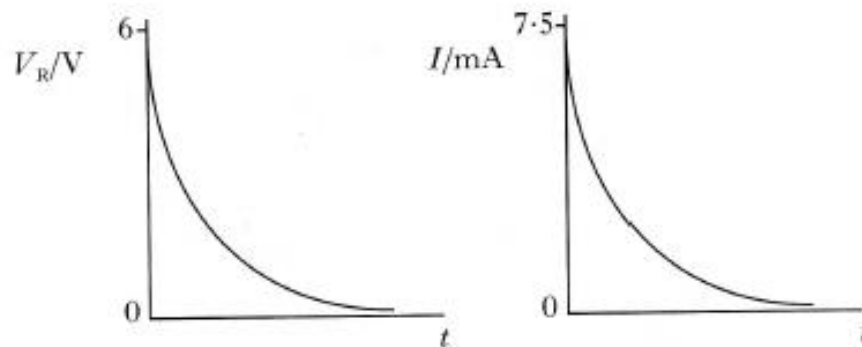The graphs below show how the potential difference V_R across the **resistor** and the current I in the circuit vary with time from the instant switch S is closed.



- | | |
|---|---|
| (i) What is the potential difference across the capacitor when it is fully charged? | 1 |
| (ii) Calculate the energy stored in the capacitor when it is fully charged. | 3 |
| (iii) Calculate the resistance of R in the circuit above. | 3 |

20 marks